


Logic Circuits II

Combinational Logic vs. Sequential Logic

- The outputs of a combinational logic circuit
 - Totally dependent on the current input values and determined by combining the input values using Boolean operations
- The outputs of a sequential logic circuit
 - Depend not only on the current input values but also on the past inputs
 - Logic gates + memory
 - Outputs are a function of the current input values and the data stored in memory
 - A function of time
 - States

Clock

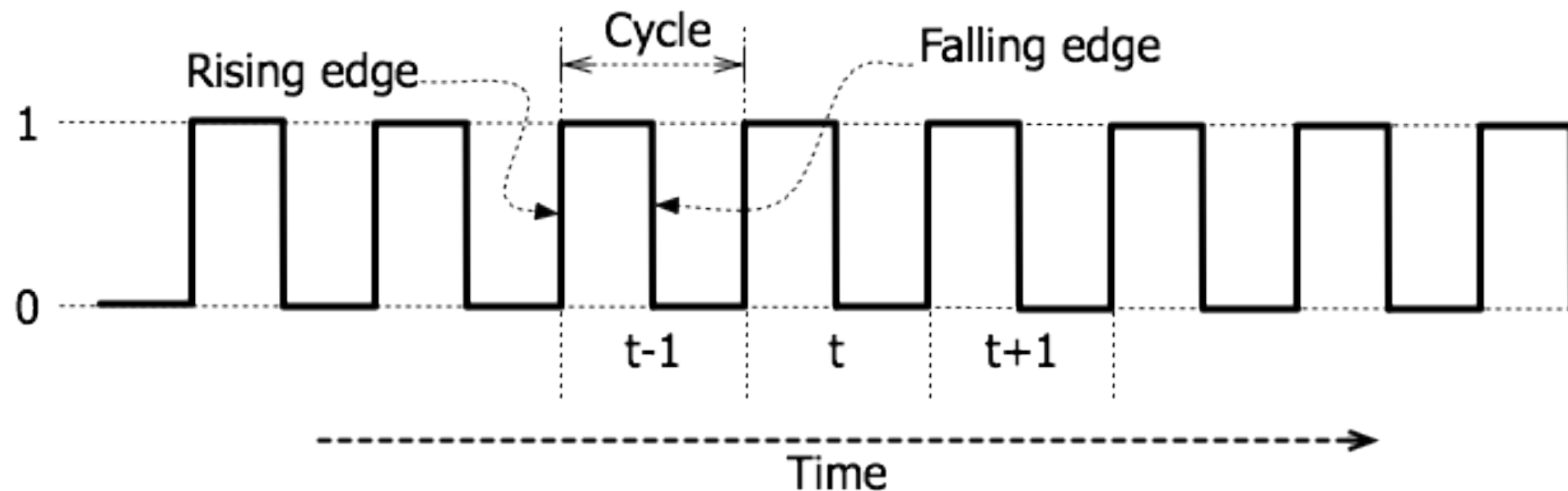- The clock signal is simultaneously broadcast to every circuit component
- Every operation in the circuit must be completed inside a clock cycle





Gate Delay

- Also known as propagation delay
- The time delay between the changes when an input change causes an output change

The SR Latch




S	R	Q
0	0	Q_{prev} (no change)
0	1	0
1	0	1
1	1	Undefined

$$Q = S \vee (R' \wedge Q_{prev})$$

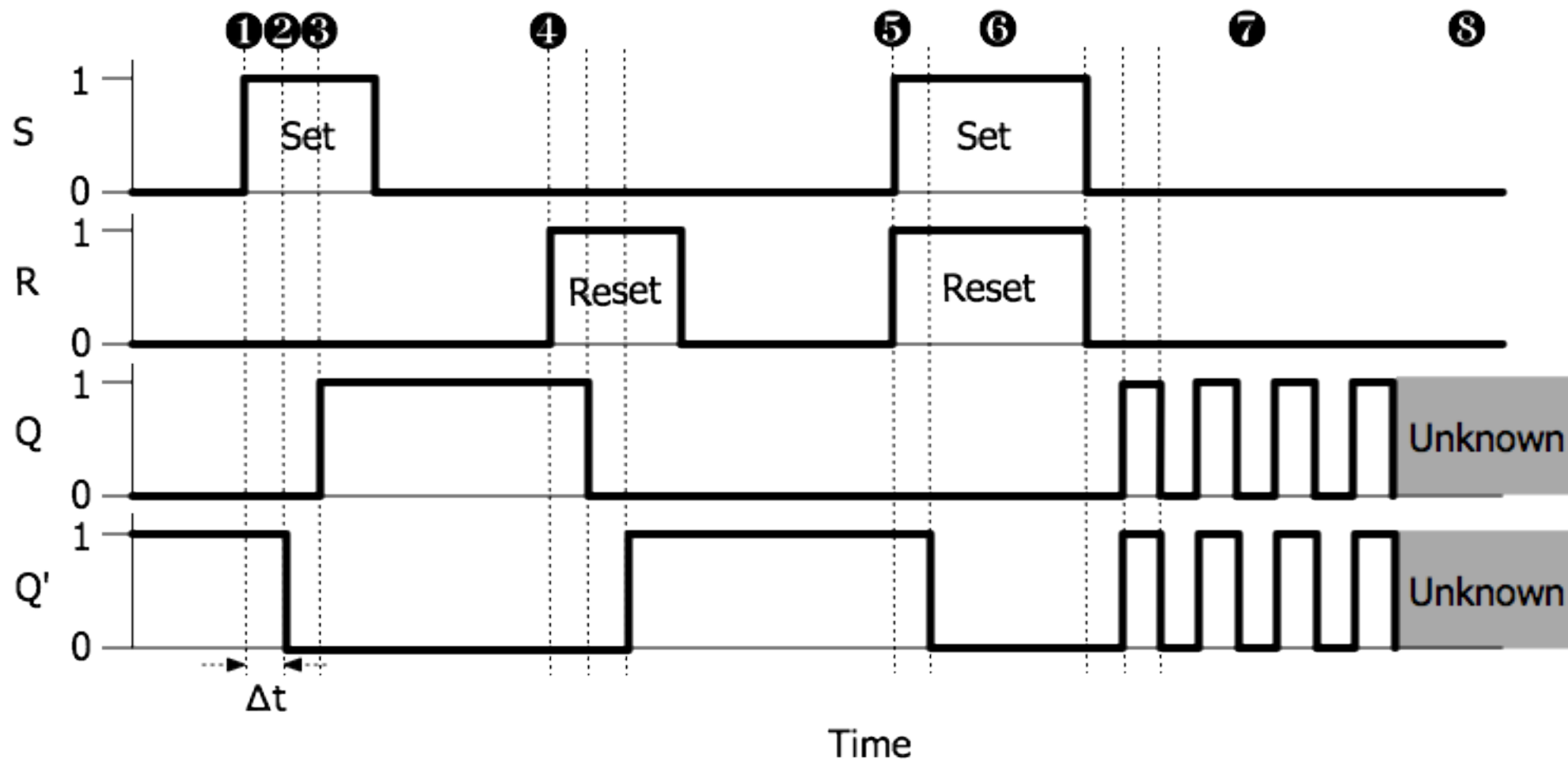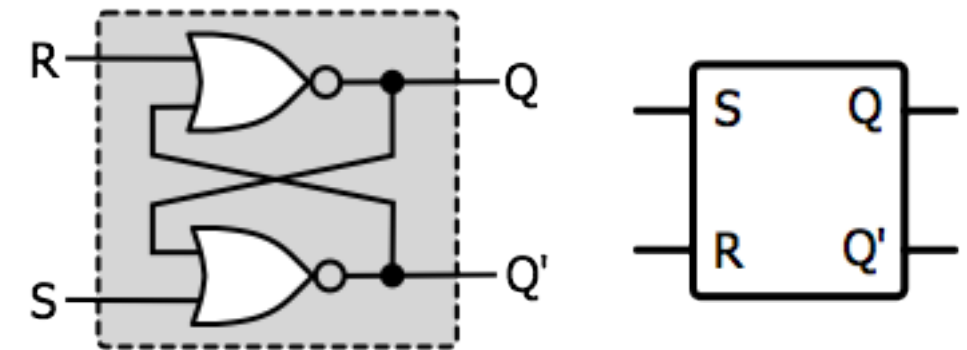

The D Latch



C	D	Q
0	X	Q_{prev} (no change)
1	0	0
1	1	1

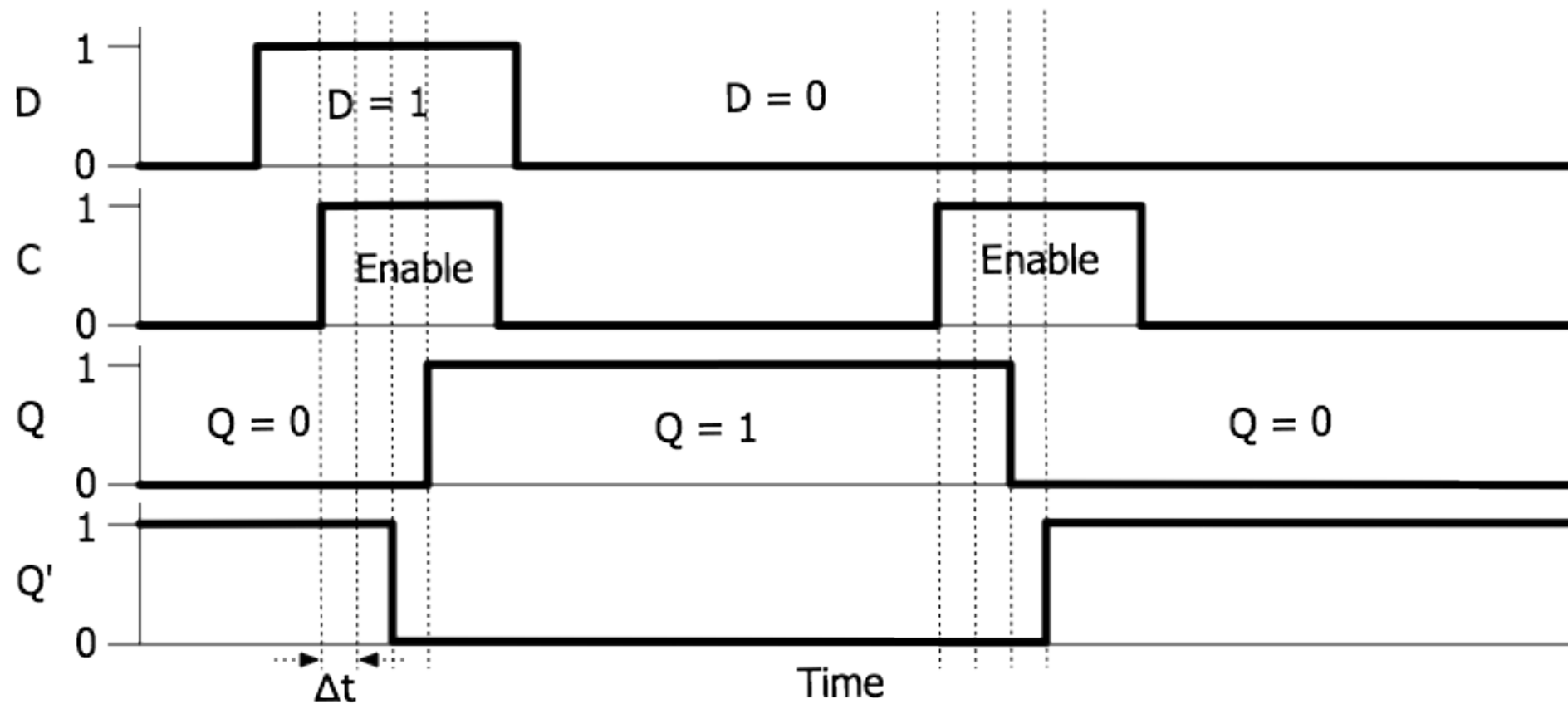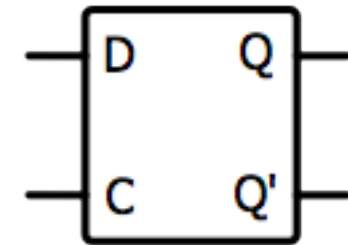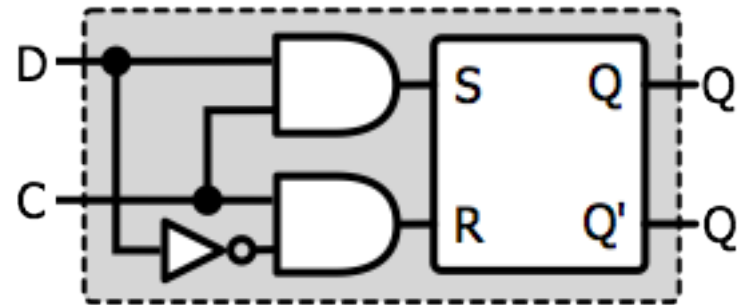


Latches vs. Flip-flops

- Latches are transparent
 - As long as the control input C remains 1, the output of the D latch will momentarily change each time its input changes
- Flip-flops are not transparent
 - The key difference between latches and flip-flops

The D Flip-flop


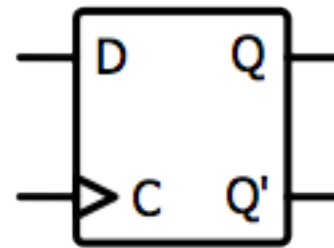
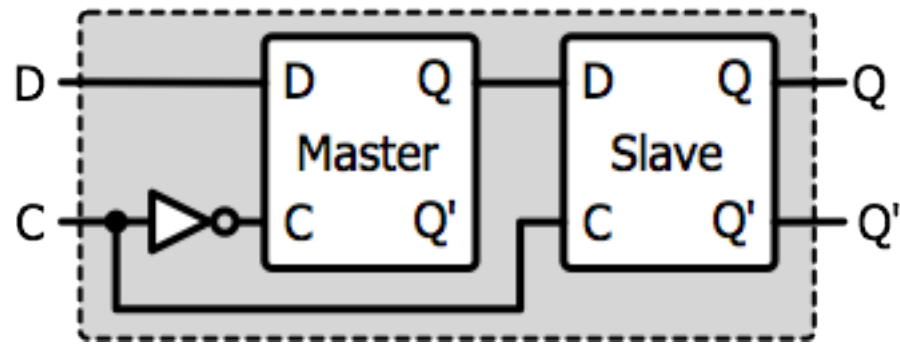


Asynchronous inputs:
preset and clear

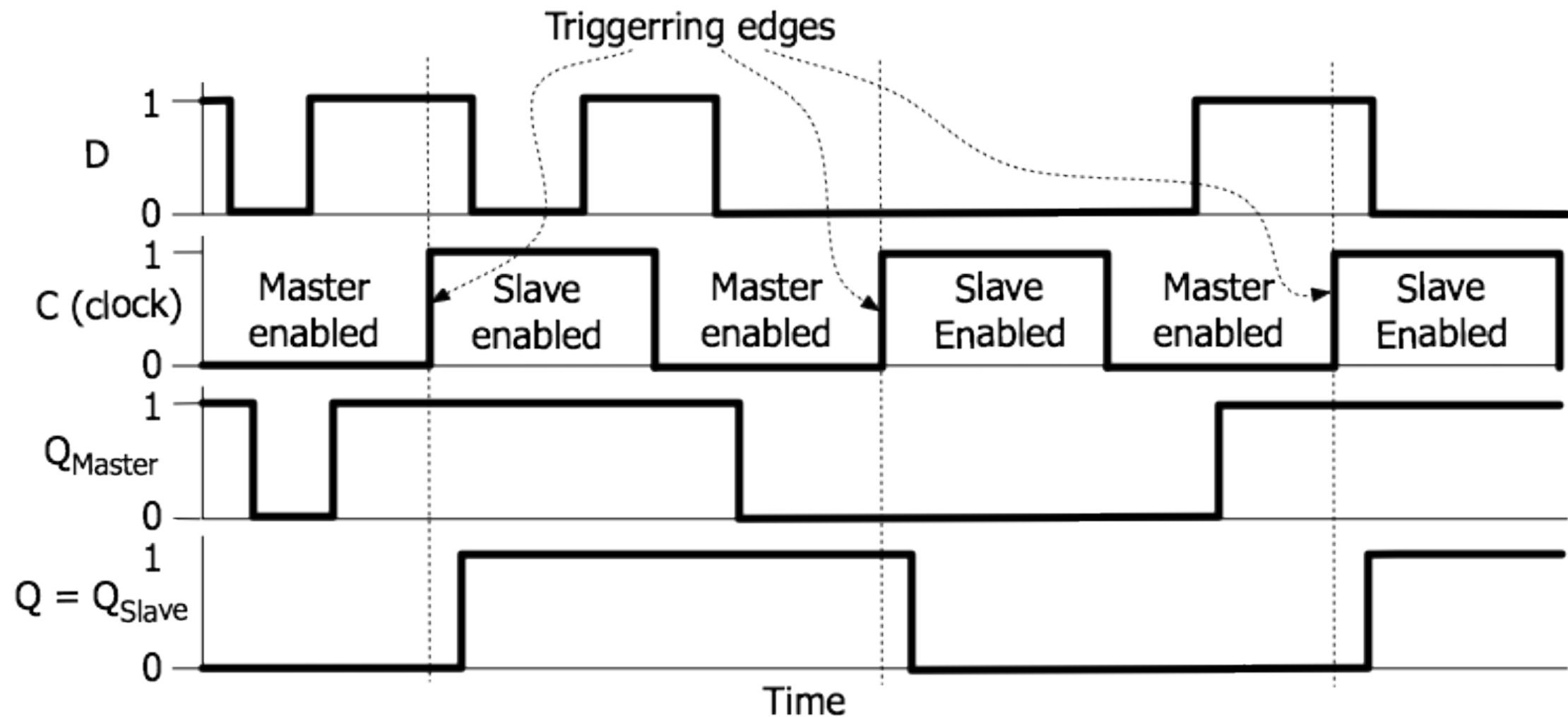

Registers

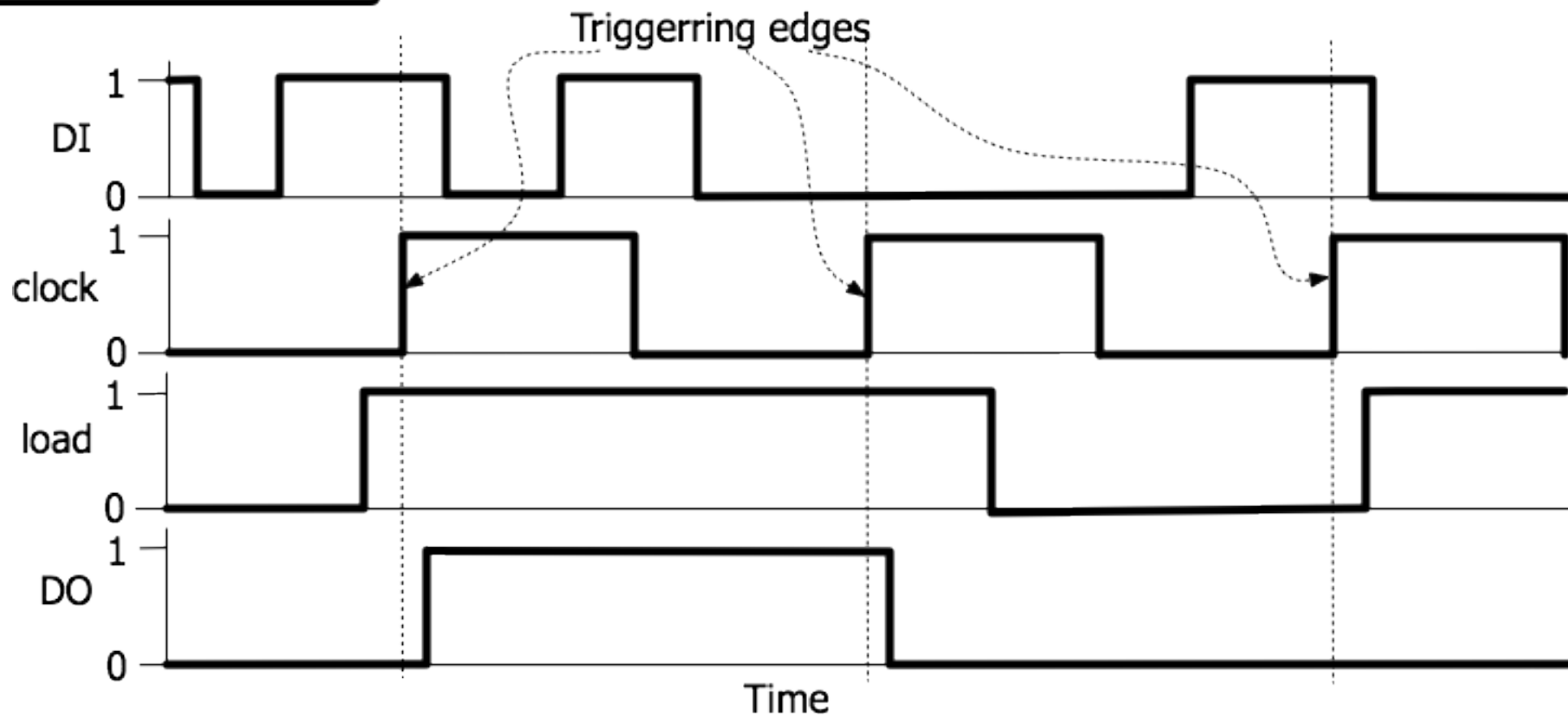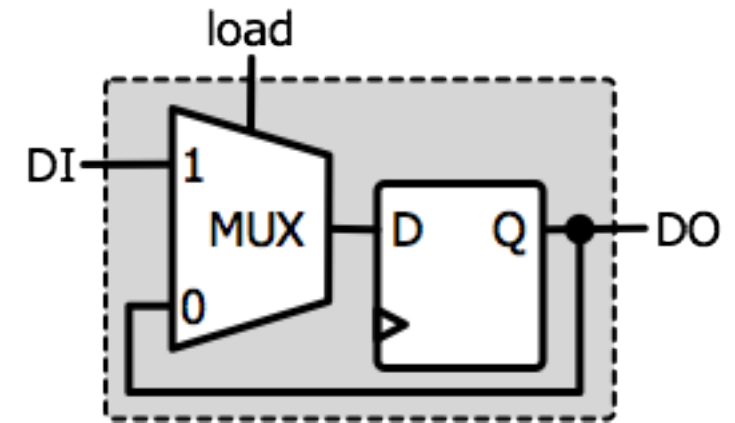
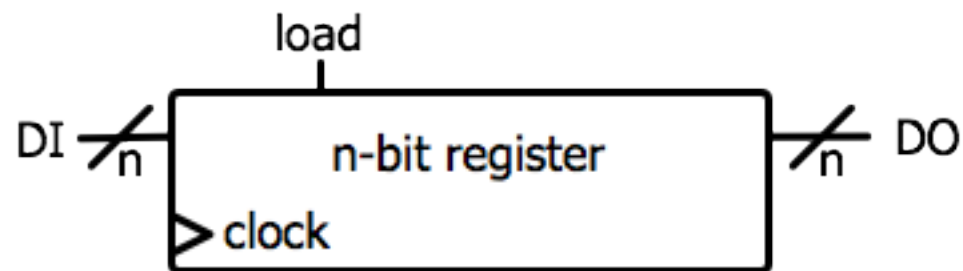
- A register is a storage device that can store binary information over time
 - It is a collection of one or more flip-flops





Binary Counters

- An n-bit counter is an n-bit register that goes through a predetermined sequence of states upon the application of the clock signal
- A counter that follows the binary number sequence is called a binary counter

Binary Counters (contd.)

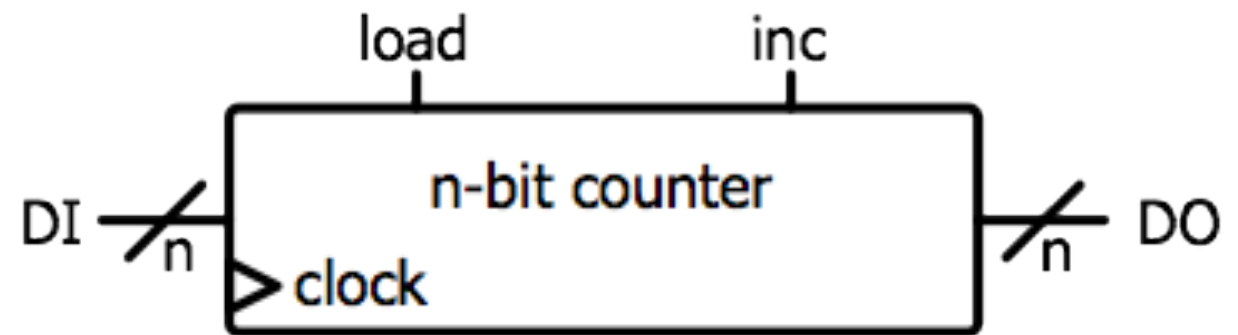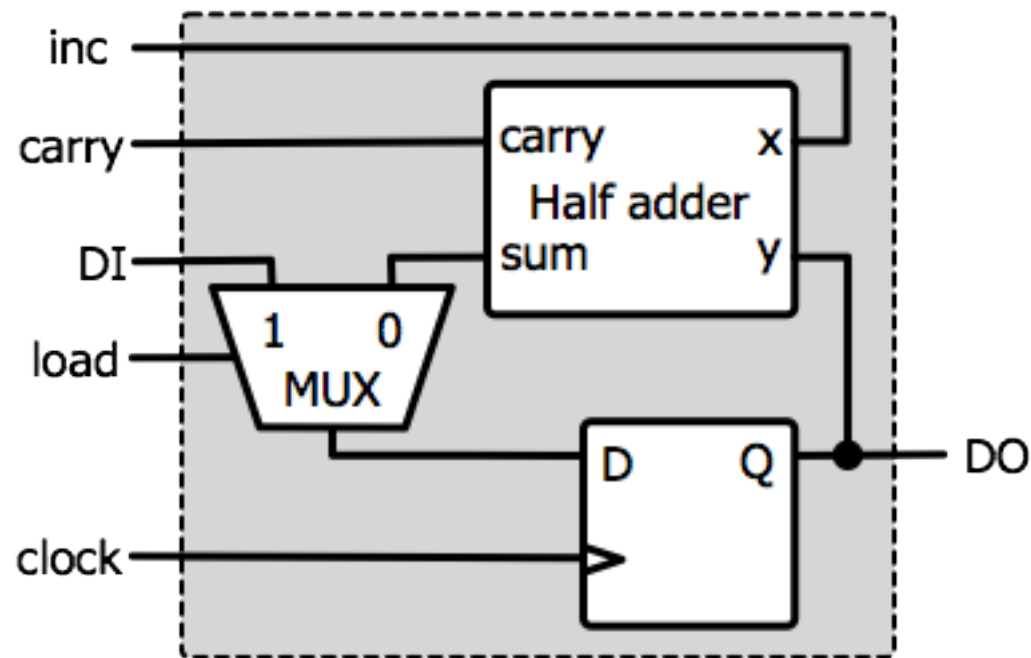


Binary Counters (contd.)

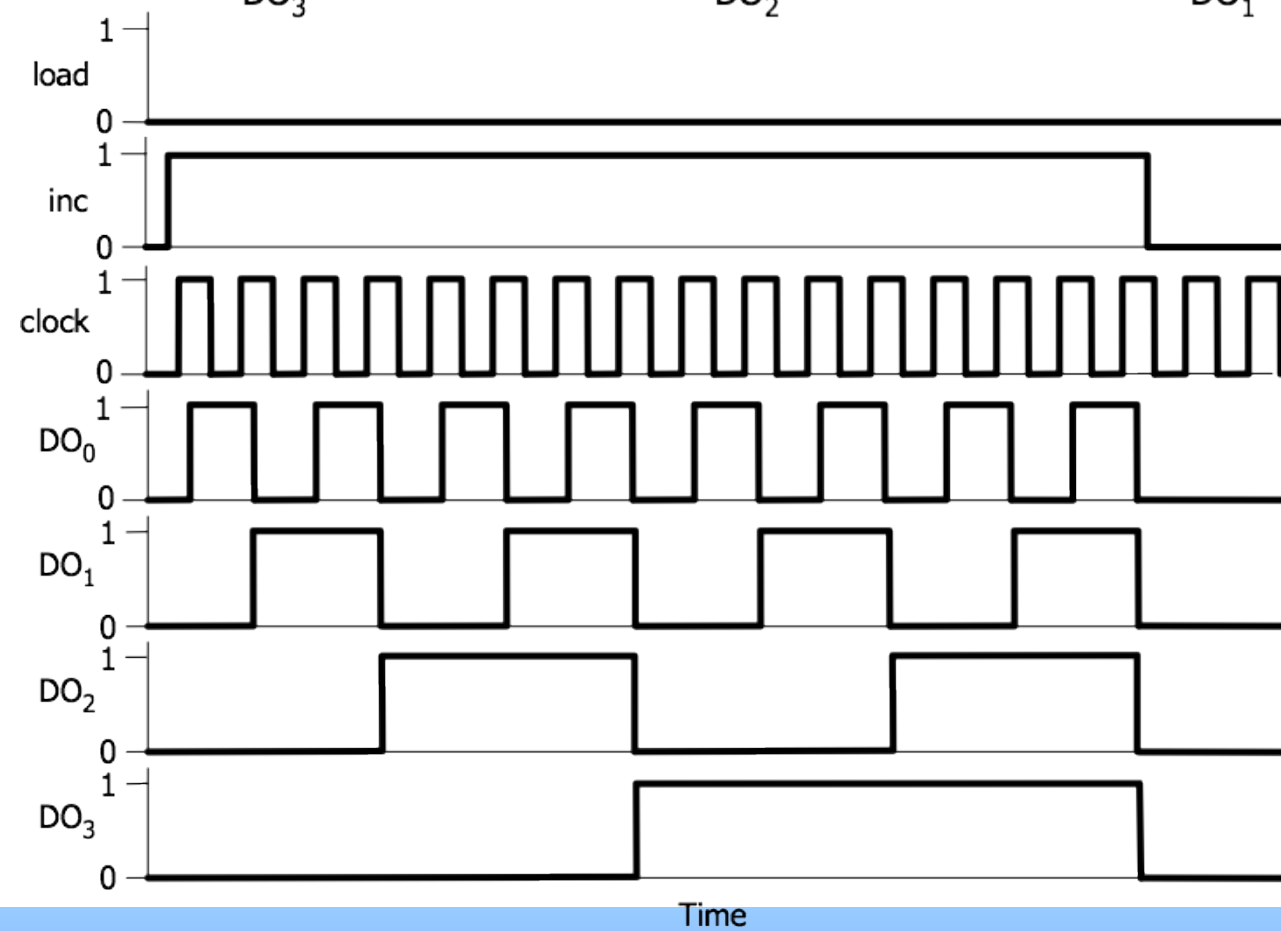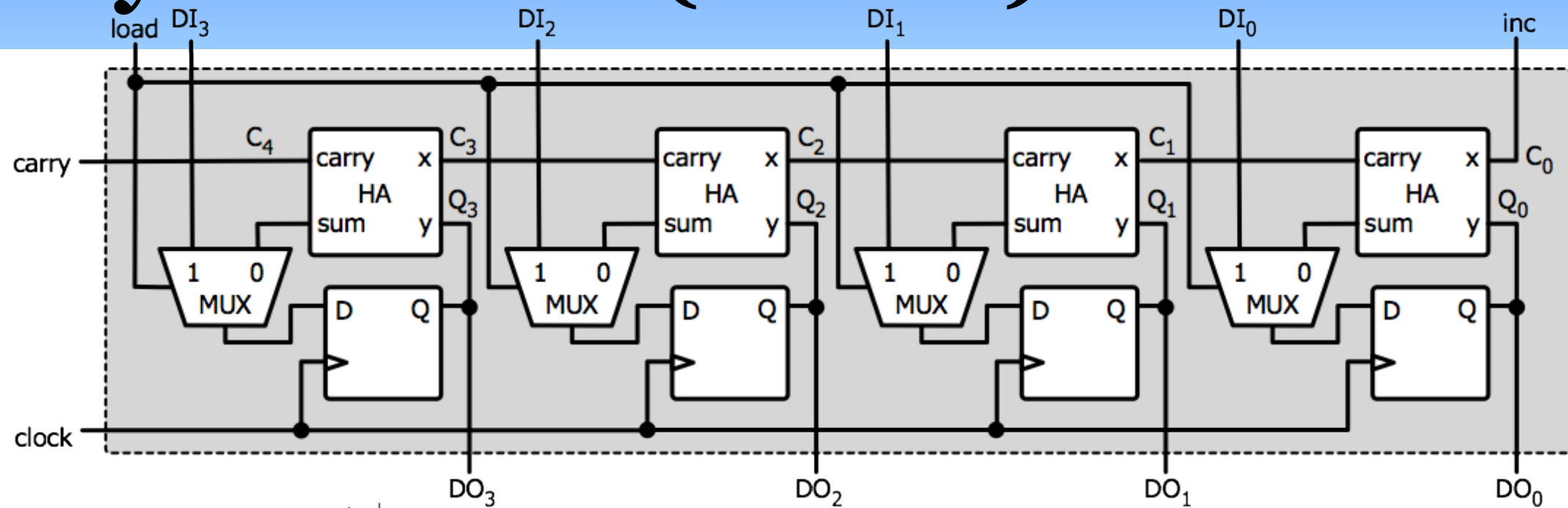

Register Files



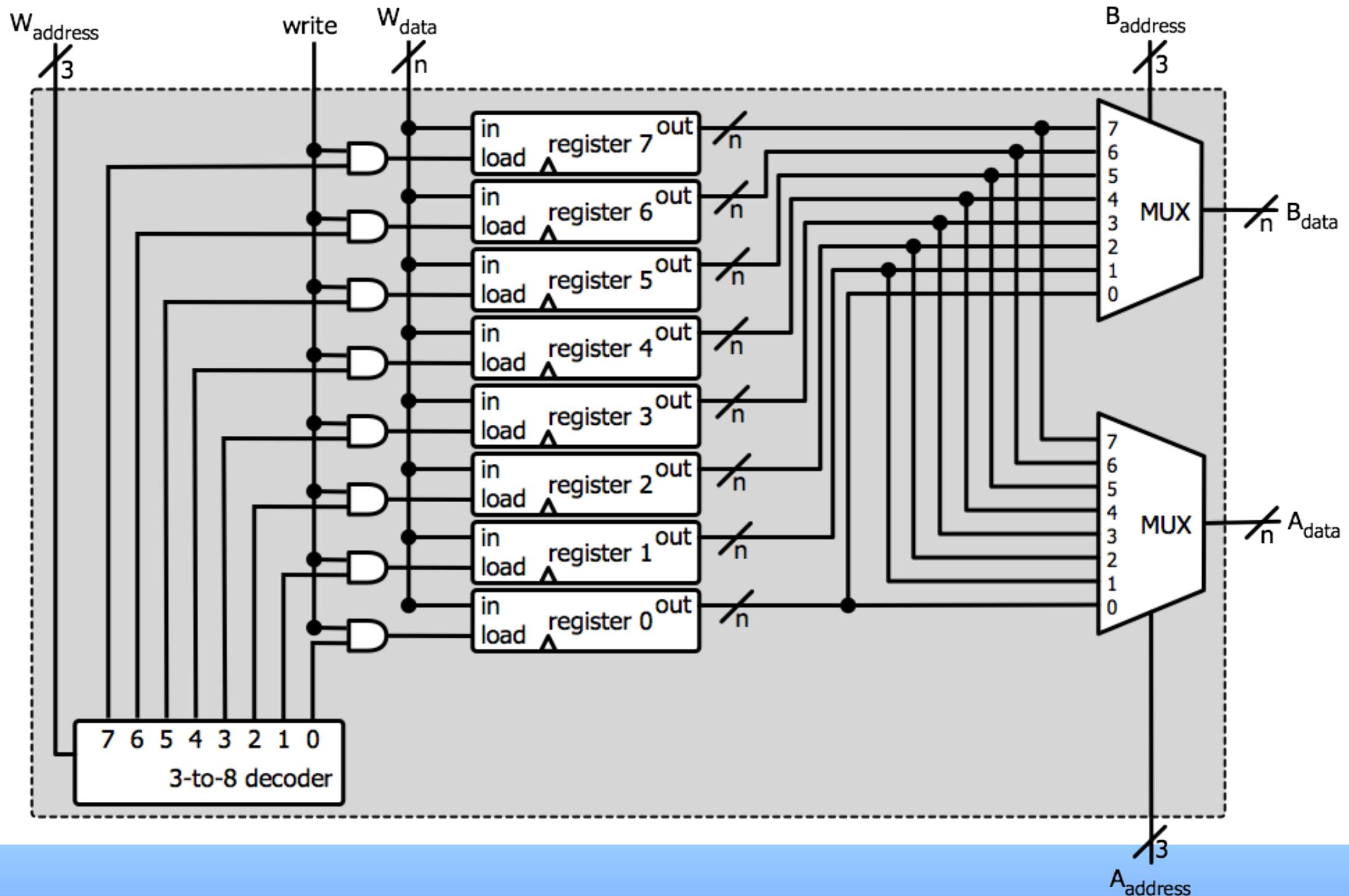
- A register file is an array of registers in a CPU



Tristate Buffers

- Also known as tristate drivers
- A third state, called a high-impedance state and denoted as Hi – Z, in addition to 0 and 1





E	D	O
0	X	Hi-Z
1	0	0
1	1	1

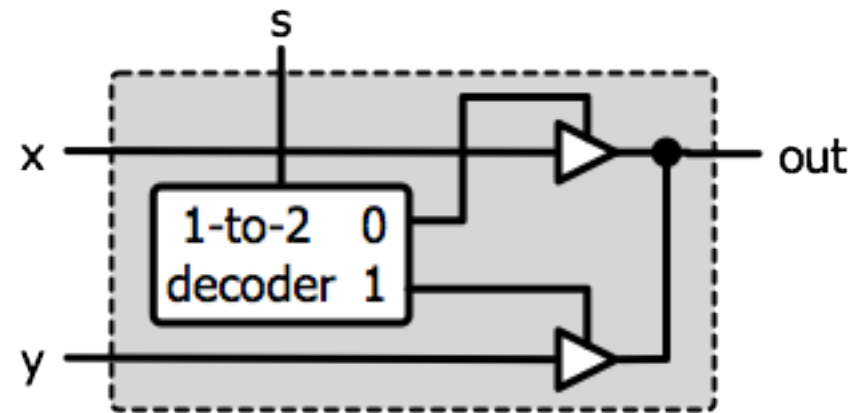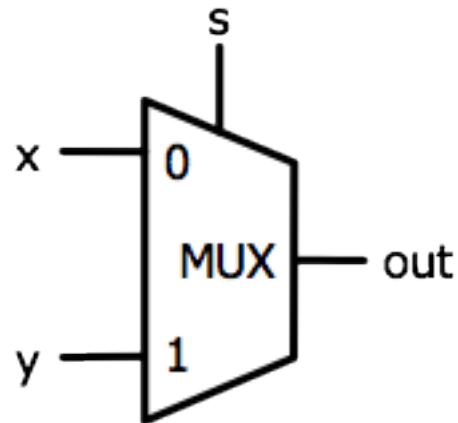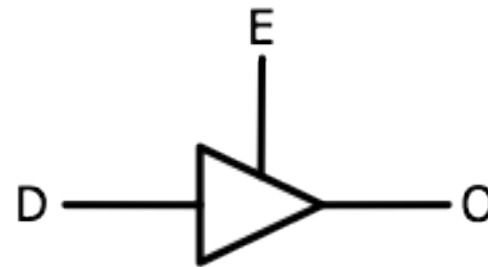


RAM

- Random access memory
- A word is a unit of information stored to and read from memory
- Able to access randomly chosen words regardless of the order in which they are accessed
- Thought as an array of 2^m w- bit registers + some access circuits to transfer information from/into it
 - Each word has a unique address


Memory Cell

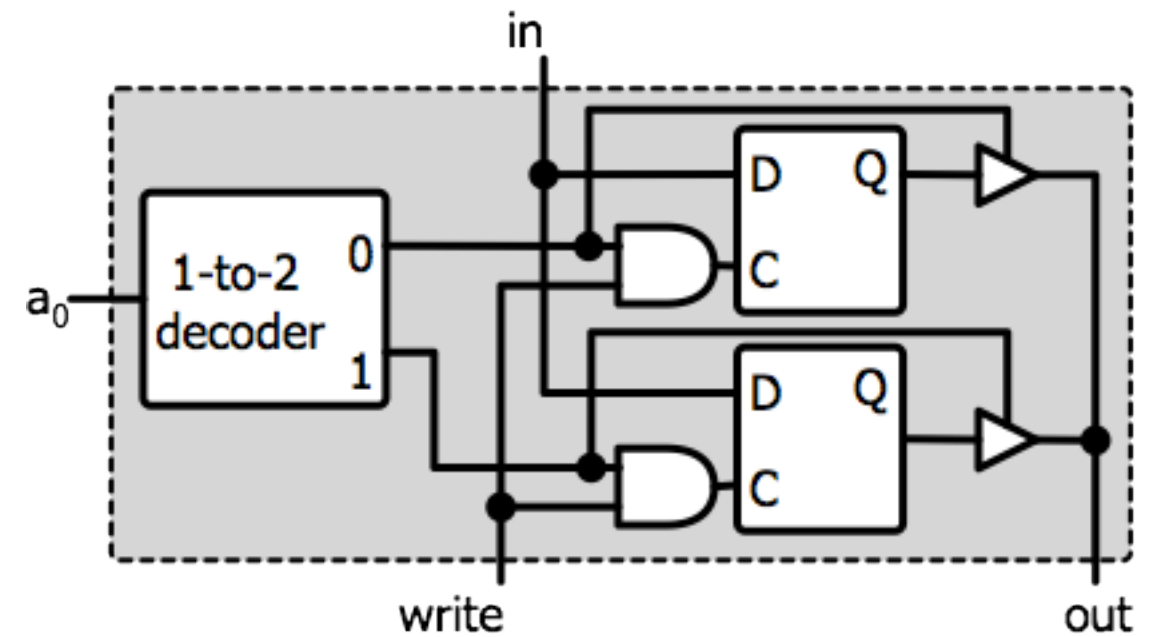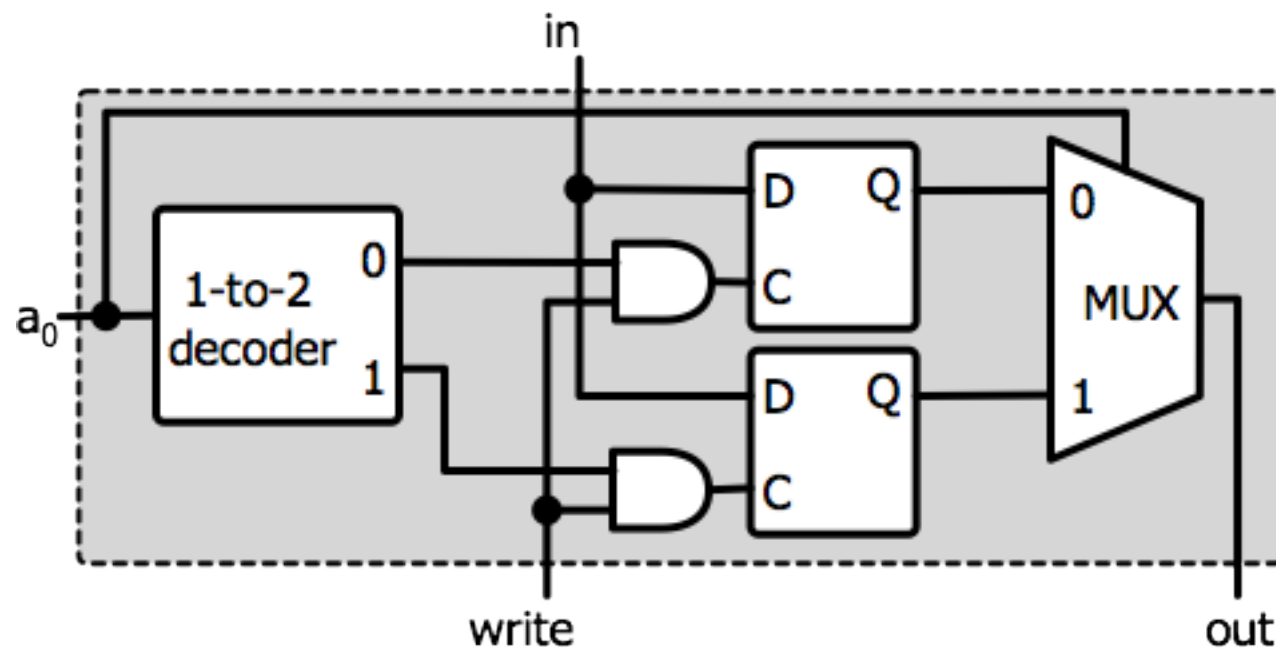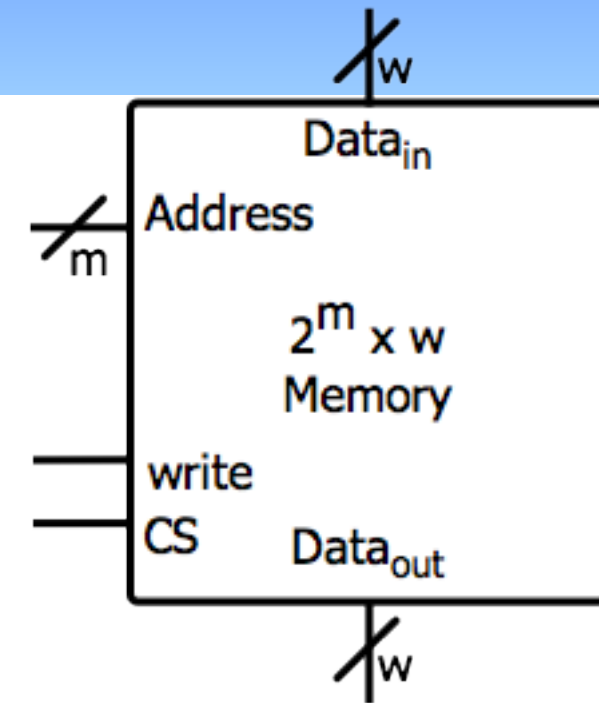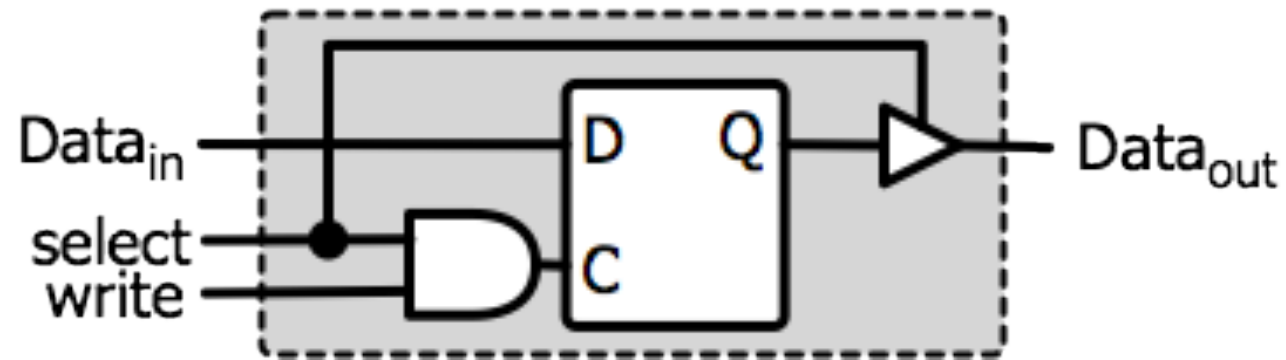


4×4 RAM

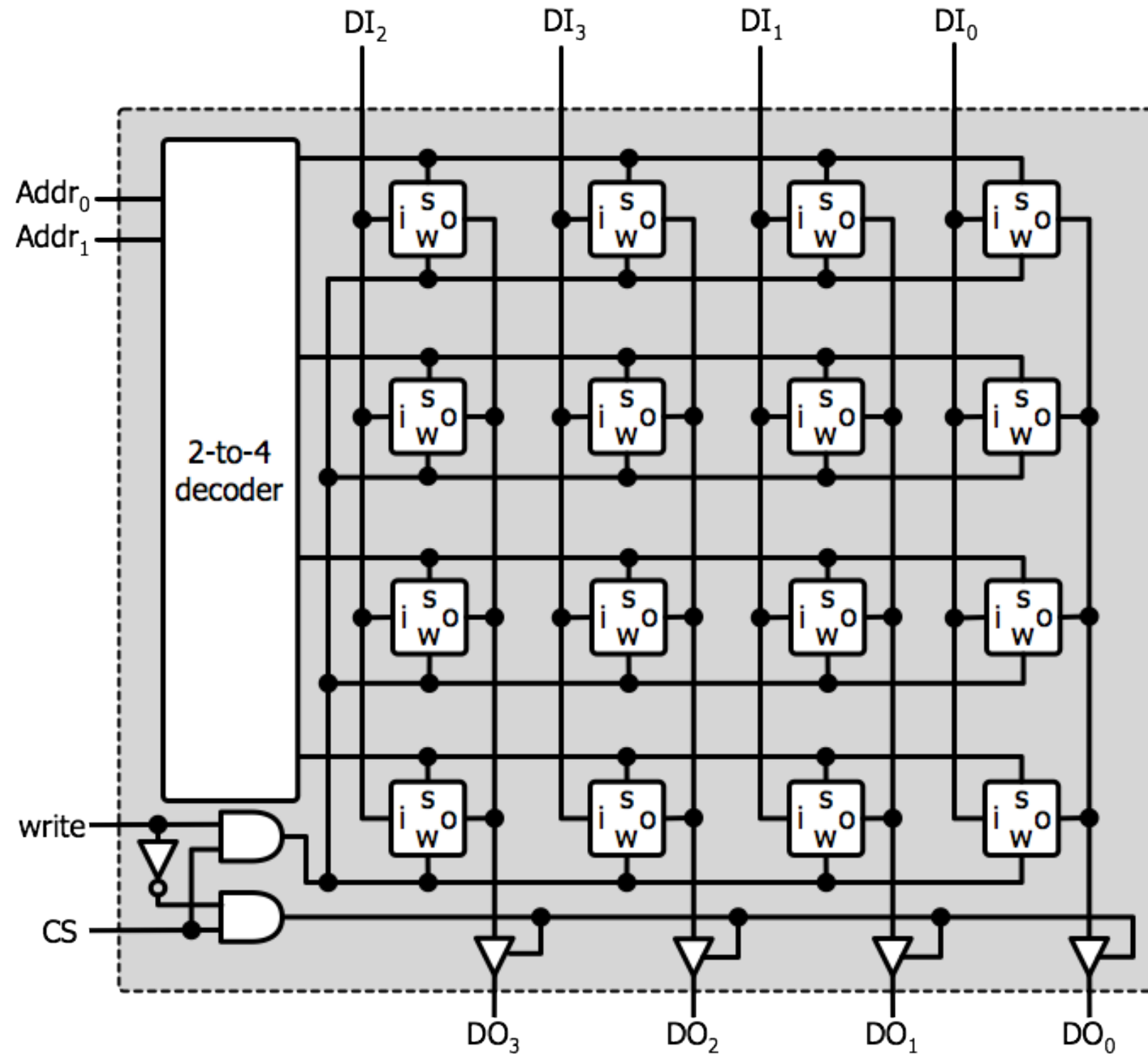

Building a RAM with Bigger Words

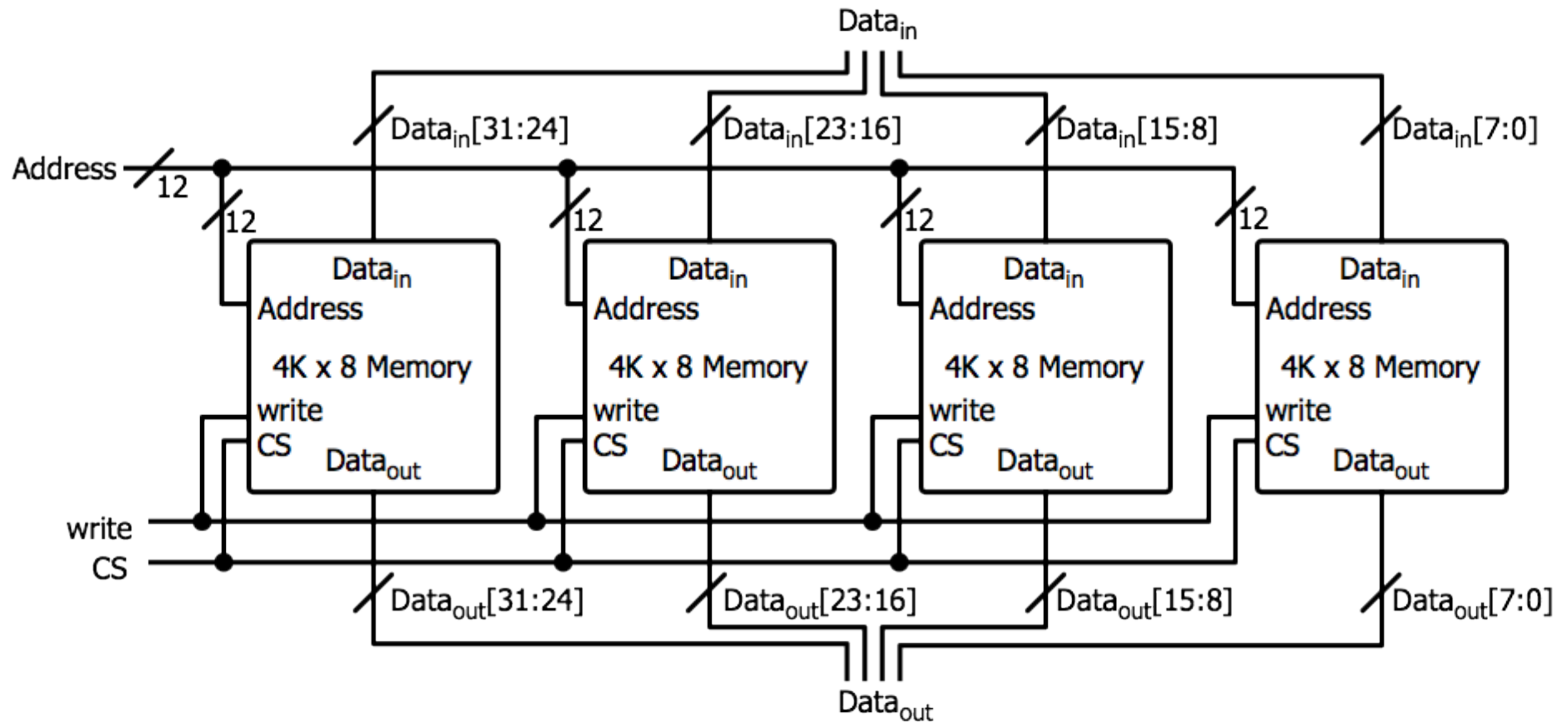


Building a RAM with More Words

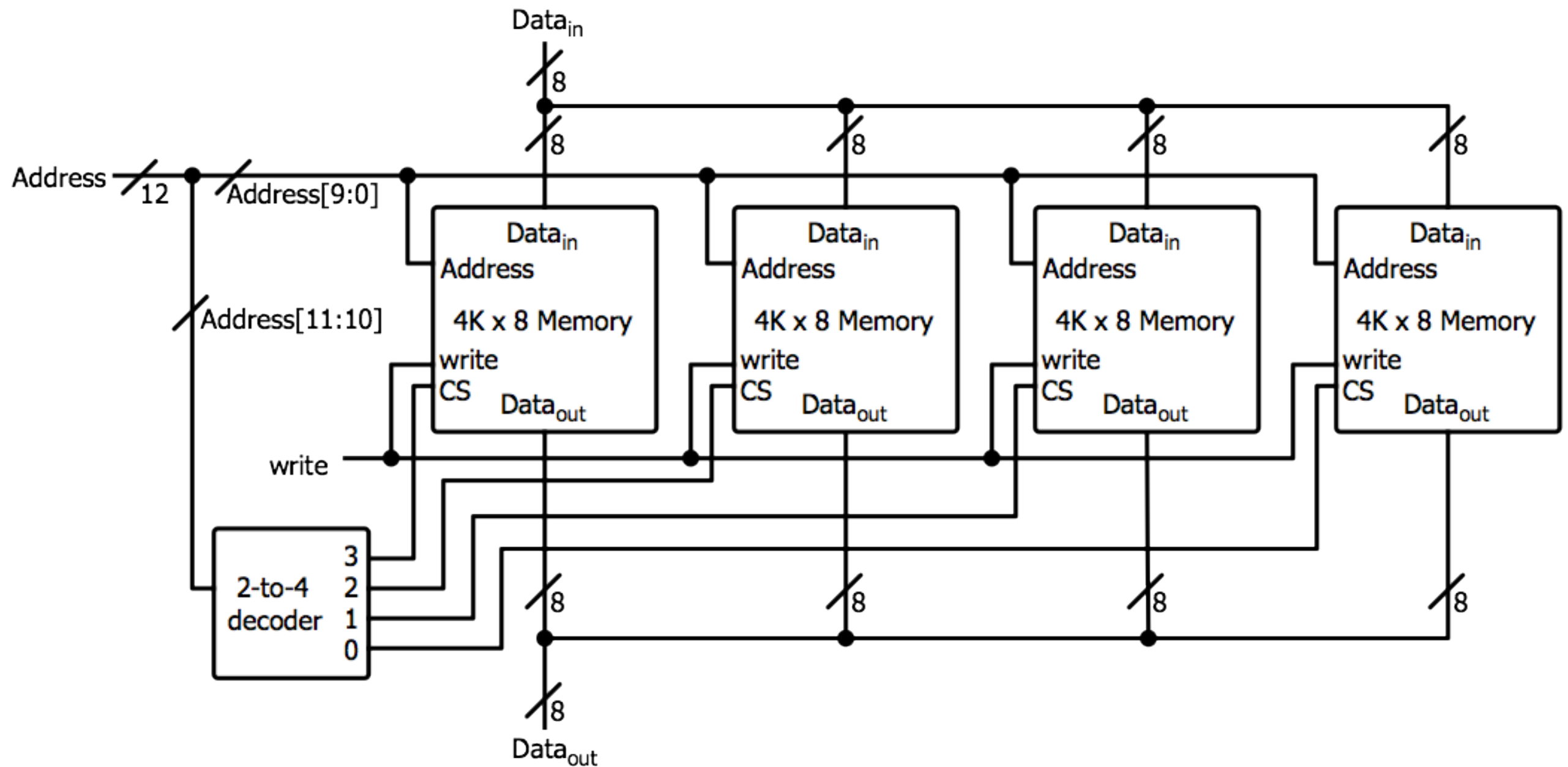

RAM Read Cycle

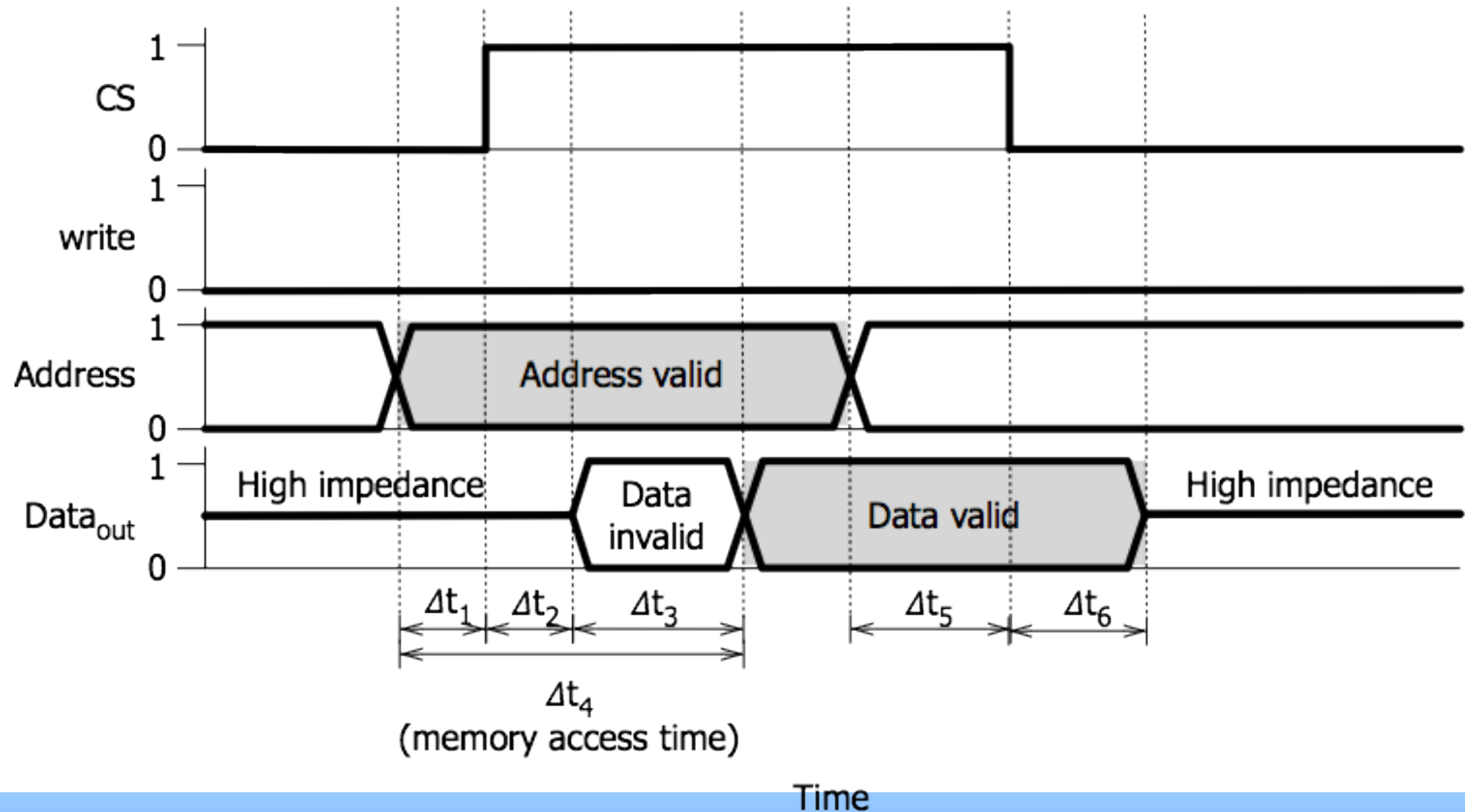- The maximum time ($\Delta t_1 + \Delta t_2 + \Delta t_3$) taken between the application of the address to address lines and the appearance of the valid data on the data output lines is called memory access time



RAM Write Cycle

